

CSE 460: VLSI Design (Lab)

Experiment 3, Part 2:
Sequential Circuits Real-life Projects
Vending Machine




Inspiring Excellence


What is Vending Machine?




What is Vending Machine?

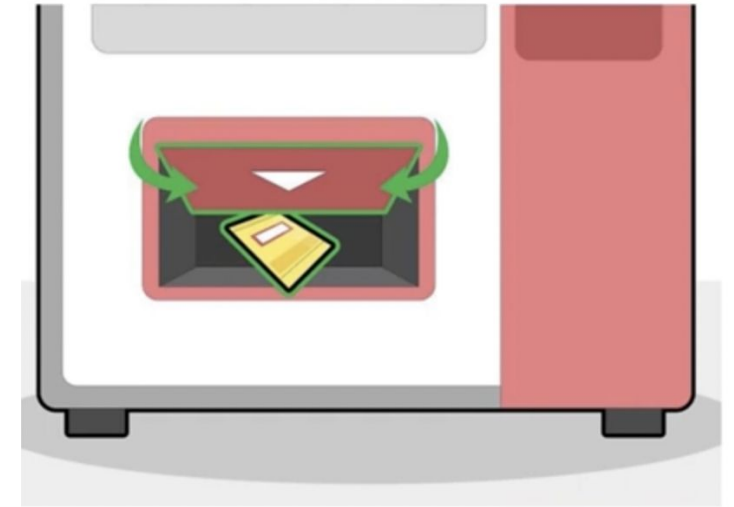


What is Vending Machine?

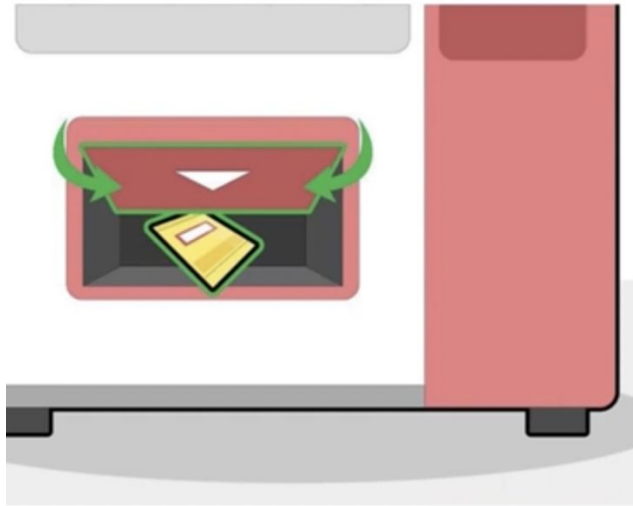


Application Description

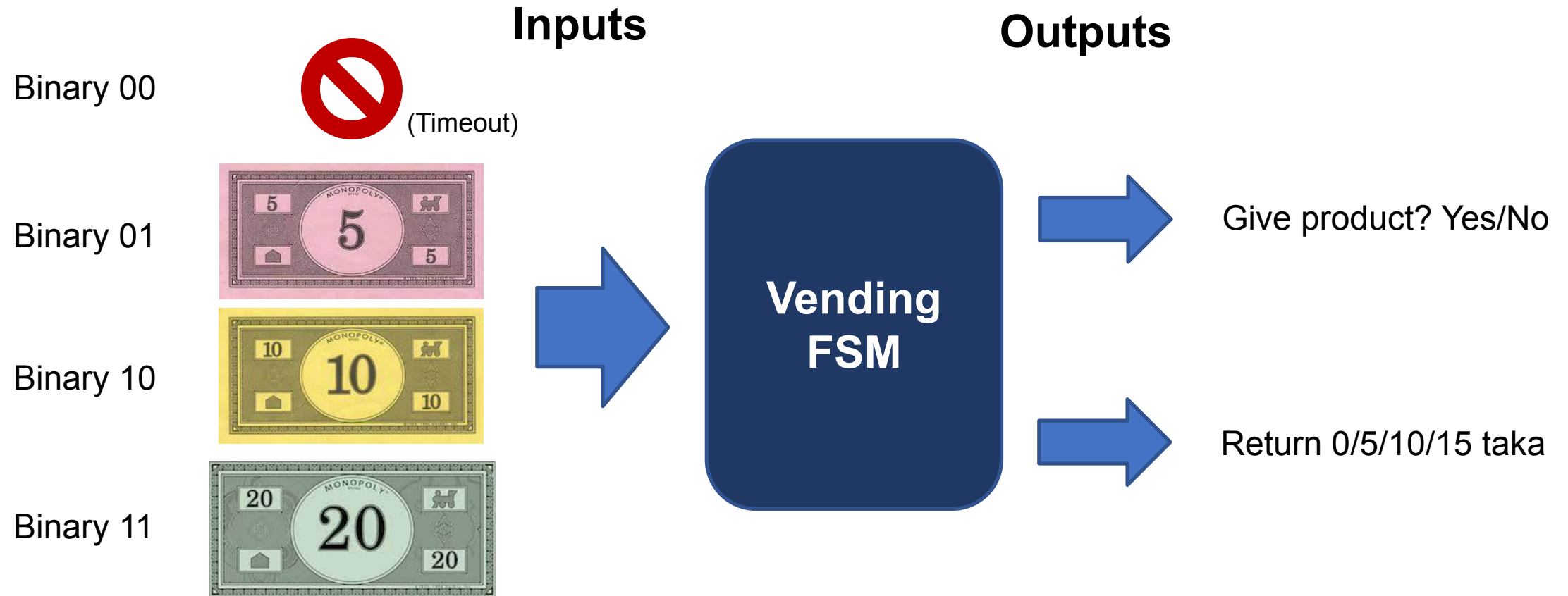

10 Tk Product Case (State Diagram)

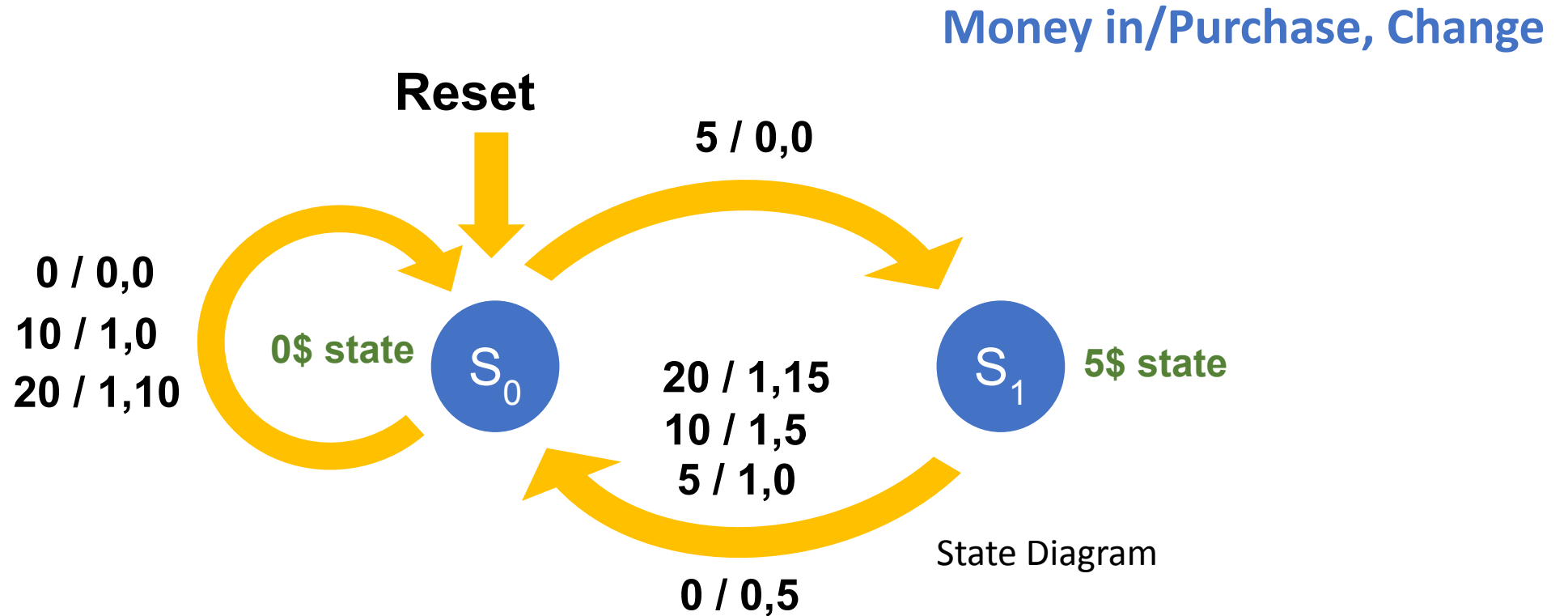

10 Tk Product Case (State Table)

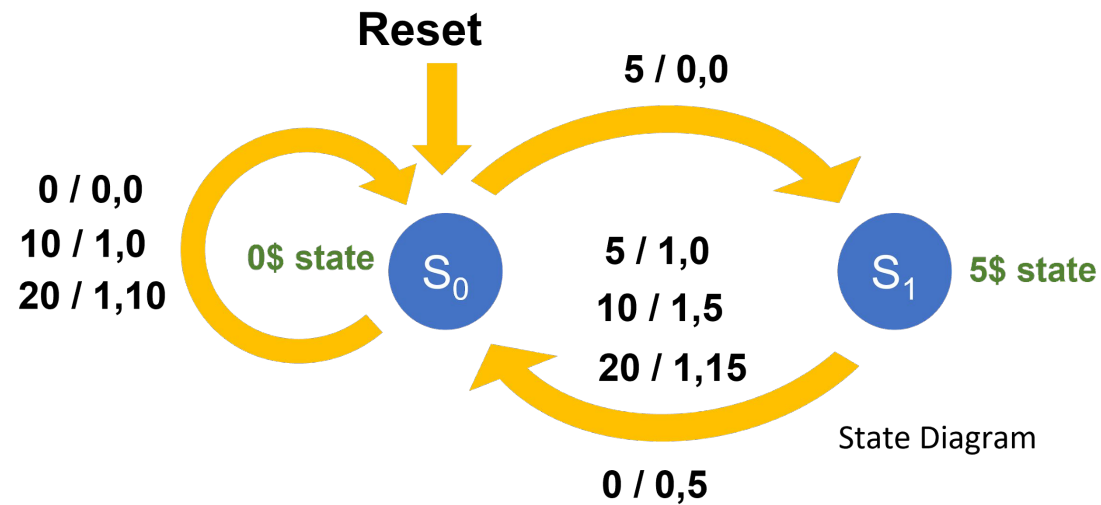

Present State	Next State				Output							
	Y_2Y_1				z				C_2C_1			
(y_2y_1)	(w_2w_1)				(w_2w_1)				$c(w_2w_1)$			
	00	01	10	11	00	01	10	11	00	01	10	11
S0	S0	S1	S0	S0	0	0	1	1	00	00	00	10
S1	S0	S0	S0	S0	0	1	1	1	01	00	01	11

State Table

Present State	Next State				Output							
	Y_2Y_1				z				C_2C_1			
(y_2y_1)	(w_2w_1)				(w_2w_1)				$c(w_2w_1)$			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	00	00	0	0	1	1	00	00	00	10
01	00	00	00	00	0	1	1	1	01	00	01	11

State Assigned Table



10 Tk Product Case (Code Snippet)

Present State (y ₂ y ₁)	Next State Y ₂ Y ₁				Output							
	Y ₂ Y ₁				z				C ₂ C ₁			
	(w ₂ w ₁)				(w ₂ w ₁)				c(w ₂ w ₁)			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	00	00	0	0	1	1	00	00	00	10
01	00	00	00	00	0	1	1	1	01	00	01	11

State Assigned Table

```
state0: if(cash_in == 2'b00)
    begin
        next_state = state0;
        purchase = 0;
        cash_return = 0;
    end
else if(cash_in == 2'b01)
    begin
        next_state=state1;
        purchase = 0;
        cash_return = 0;
    end
else if(cash_in == 2'b10)
    begin
        next_state=state0;
        purchase=1;
        cash_return=0;
    end
else if(cash_in == 2'b11)
    begin
        next_state = state0;
        purchase = 1;
        cash_return = 2'b10;
    end
end
```



10 Tk Product Case (Code Snippet)

Present State (y ₂ y ₁)	Next State Y ₂ Y ₁				Output							
	Y ₂ Y ₁				z				C ₂ C ₁			
	(w ₂ w ₁)				(w ₂ w ₁)				c(w ₂ w ₁)			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	00	00	0	0	1	1	00	00	00	10
01	00	00	00	00	0	1	1	1	01	00	01	11


State Assigned Table

```
state1: if (cash_in == 2'b00)
begin
    next_state = state0;
    purchase = 0;
    cash_return = 2'b01;
end
else if (cash_in == 2'b01)
begin
    next_state = state0;
    purchase = 1;
    cash_return = 0;
end
else if (cash_in == 2'b10)
begin
    next_state = state0;
    purchase = 1;
    cash_return = 2'b01;
end
else if (cash_in == 2'b11)
begin
    next_state = state0;
    purchase = 1;
    cash_return = 2'b11;
end
endcase


always @(posedge rst, posedge clk)
if (rst == 1)
    current_state <= state0;
else
    current_state <= next_state;
endmodule
```



15 Tk Product Case (State Diagram)

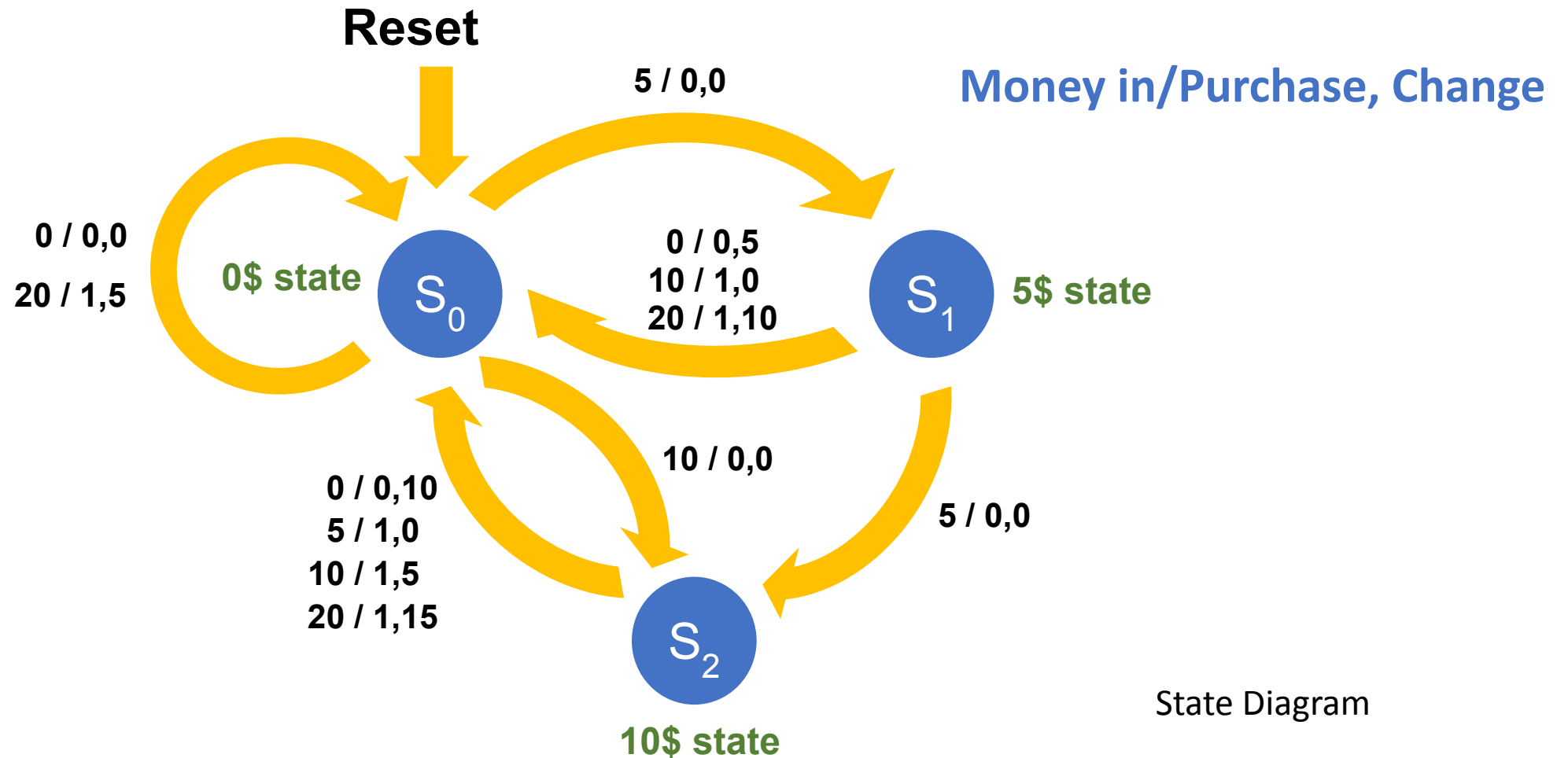

15 Tk Product Case (State Table)

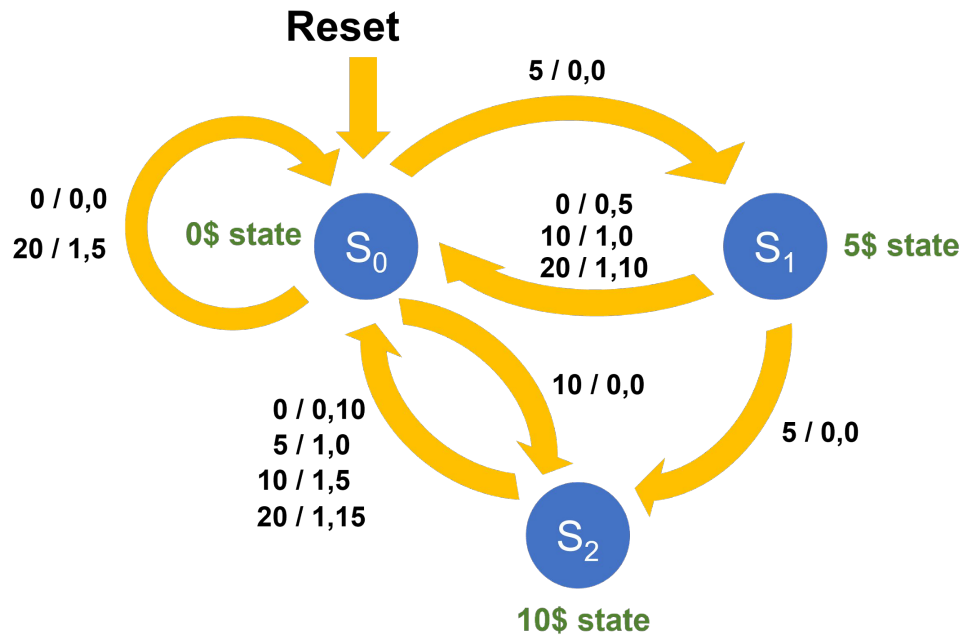

Present State	Next State				Output							
	Y ₂ Y ₁				z				C ₂ C ₁			
	(y ₂ y ₁)				(w ₂ w ₁)				c(w ₂ w ₁)			
	00	01	10	11	00	01	10	11	00	01	10	11
S ₀	S ₀	S ₁	S ₂	S ₀	0	0	0	1	00	00	00	01
S ₁	S ₀	S ₂	S ₀	S ₀	0	0	1	1	01	00	00	10
S ₂	S ₀	S ₀	S ₀	S ₀	0	1	1	1	10	00	01	11

State Table

15 Tk Product Case (State Assigned Table)

Present State	Next State				Output							
	Y_2Y_1				z				C_2C_1			
(y_2y_1)	(w_2w_1)				(w_2w_1)				$c(w_2w_1)$			
	00	01	10	11	00	01	10	11	00	01	10	11
S_0	S_0	S_1	S_2	S_0	0	0	0	1	00	00	00	01
S_1	S_0	S_2	S_0	S_0	0	0	1	1	01	00	00	10
S_2	S_0	S_0	S_0	S_0	0	1	1	1	10	00	01	11

State Table

Present State	Next State				Output							
	Y_2Y_1				z				C_2C_1			
(y_2y_1)	(w_2w_1)				(w_2w_1)				(w_2w_1)			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	10	00	0	0	0	1	00	00	00	01
01	00	10	00	00	0	0	1	1	01	00	00	10
10	00	00	00	00	0	1	1	1	10	00	01	11
11	d	d	d	d	d	d	d	d	d	d	d	d

State Assigned Table



15 Tk Product Case (Code Snippet)

Present State	Next State				Output							
	Y ₂ Y ₁				z				C ₂ C ₁			
(y ₂ y ₁)	(w ₂ w ₁)				(w ₂ w ₁)				(w ₂ w ₁)			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	10	00	0	0	0	1	00	00	00	01
01	00	10	00	00	0	0	1	1	01	00	00	10
10	00	00	00	00	0	1	1	1	10	00	01	11
11	d	d	d	d	d	d	d	d	d	d	d	d

State Assigned Table

```
state0: if(cash_in == 2'b00)
    begin
        next_state = state0;
        purchase = 0;
        cash_return = 0;
    end
else if(cash_in == 2'b01)
    begin
        next_state = state1;
        purchase = 0;
        cash_return = 0;
    end
else if(cash_in == 2'b10)
    begin
        next_state = state2;
        purchase = 0;
        cash_return = 0;
    end
else if(cash_in == 2'b11)
    begin
        next_state = state0;
        purchase = 1;
        cash_return = 2'b01;
    end
end
```



15 Tk Product Case (Code Snippet)

Present State	Next State				Output							
	Y ₂ Y ₁				z				C ₂ C ₁			
(y ₂ y ₁)	(w ₂ w ₁)				(w ₂ w ₁)				(w ₂ w ₁)			
	00	01	10	11	00	01	10	11	00	01	10	11
00	00	01	10	00	0	0	0	1	00	00	00	01
01	00	10	00	00	0	0	1	1	01	00	00	10
10	00	00	00	00	0	1	1	1	10	00	01	11
11	d	d	d	d	d	d	d	d	d	d	d	d

State Assigned Table


```

state2: if(cash_in == 2'b00)
    begin
        next_state = state0;
        purchase = 0;
        cash_return = 2'b10;
    end
else if(cash_in == 2'b01)
    begin
        next_state = state0;
        purchase = 1;
        cash_return = 0;
    end
else if(cash_in == 2'b10)
    begin
        next_state = state0;
        purchase = 1;
        cash_return = 2'b01;
    end
else if(cash_in == 2'b11)
    begin
        next_state = state0;
        purchase = 1;
        cash_return = 2'b11;
    end

```



20 Tk Product Case (State Diagram)

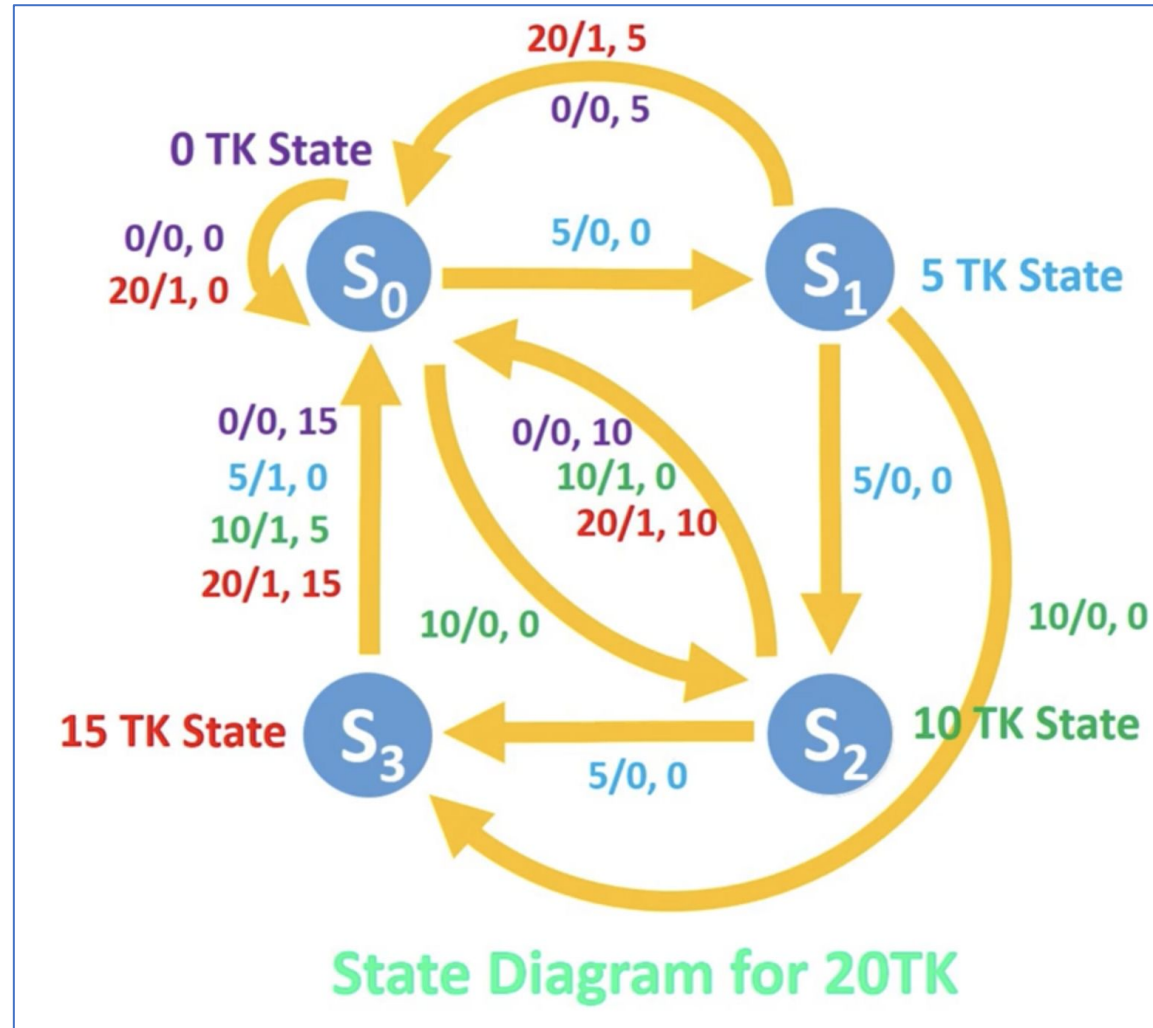

Thank you!



Inspiring Excellence

7/1/2022

CSE 460: VLSI Design

17