

CSE460: VLSI Design

Name- Ms Rodsy Tahmid

ID- 20101021

Section- 07

## Lab Assignment 4

### General guidelines

Draw the layout using the appropriate tool as taught in the lab, perform **DRC** and rectify all design errors (if any), submit the full screen screenshots of the design file and the simulation file **with proper discussion**.

#### **Problem:**

Draw the layout in *microwind2* for the logic function described the following equation:


$$Y = \overline{A.B + C}$$


Answer:

$$Y = \overline{A \cdot B + C}$$

$\downarrow$        $\downarrow$   
 AND      OR  
 └────────┘  
 NOT

$$(A + B)C$$

 


 


S/D S/D → series

S/P D/S → parallel

Circuit in microwind2:

 

### Simulation in microwind2:

 

Discussion:

Lab Assignment - 4

$$Y = \overline{A \cdot B} + C$$

Truth Table:

A	B	C	Output, Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$A \cdot B = X$$

AND		X
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

$$X + C = Z$$

OR		Z	Y
X	C	Z	Y
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Rearrangement according to Microwind Timing Diagram :

A	B	C	Output, Y
0	0	0	1
1	0	0	1
0	1	0	1
1	1	0	0
0	0	1	0
1	0	1	0
0	1	1	0
1	1	1	0

If we observe closely, we can see that the above Truth table matches the timing diagram/simulation of microwind2 i.e., the timing diagram matches the output. When  $A=B=C=0$ , Output  $Y=1$  and when  $A=B=C=1$ , Output  $Y=0$  which match the table.